
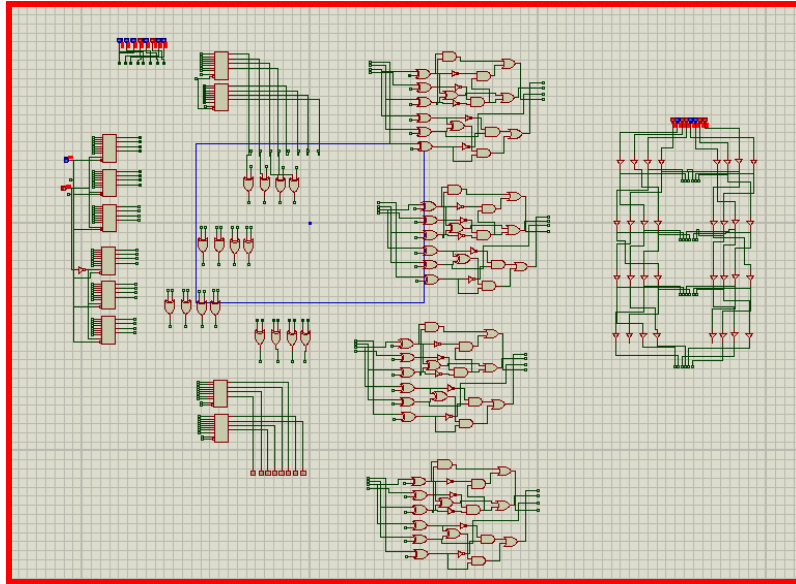


DIGISIM-PS-1


Combinational Approach

 

Input





Permutation

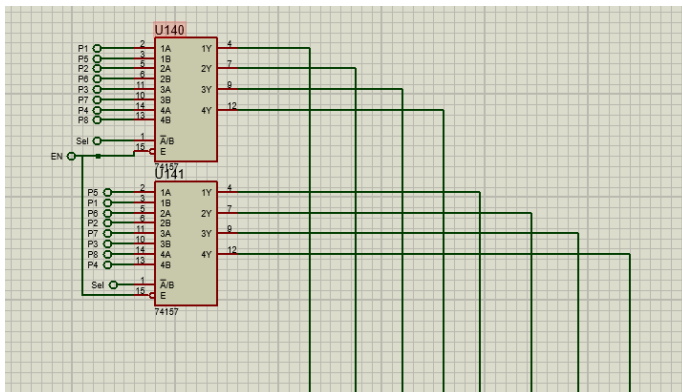


- In this part multiplexer is used for Swapping purpose of R4 and L4 In decryption .
- In encryption the Sel bit will be 0 and in Decryption Sel bit will be 1 .
- Then the output going forward with permutations given in PS .


Permuted text data

  

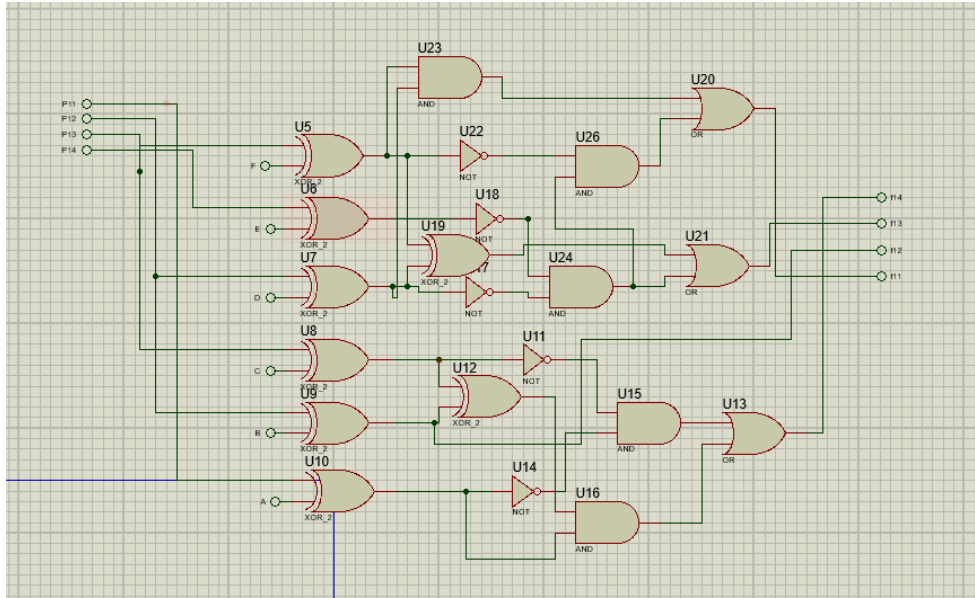
⇒ This is four step xor of left four bits with the output of function of right four bit and 6 bit generated round Key .



 
This is combinational circuit for the function in between LSB 4 bits and 6 bit round key .



⇒ This is four step round key generation

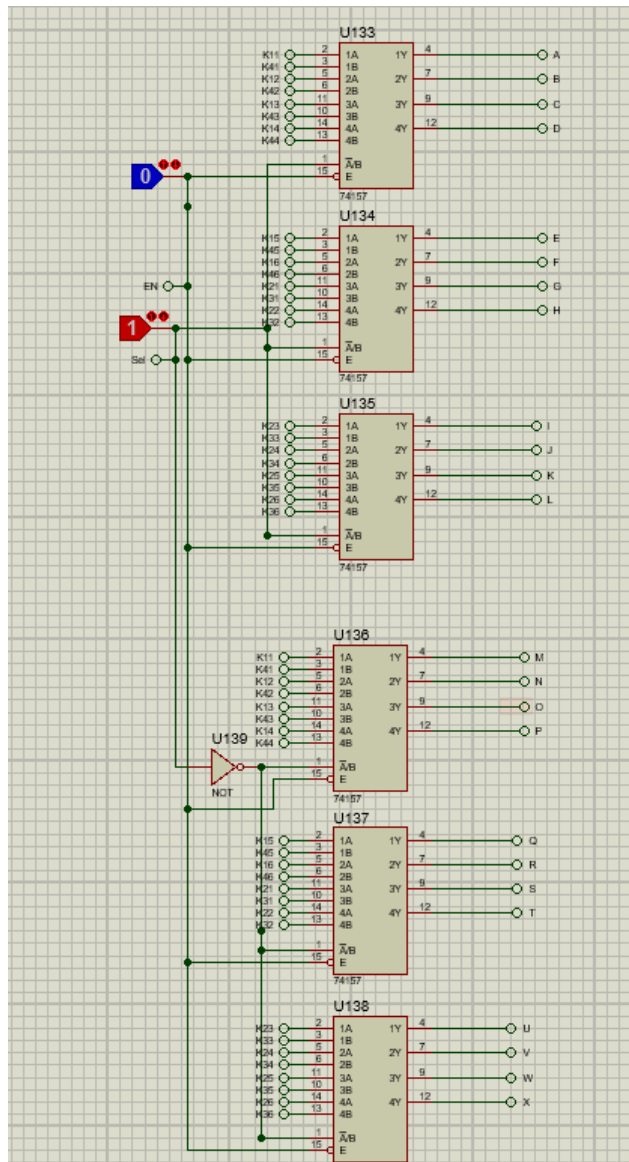


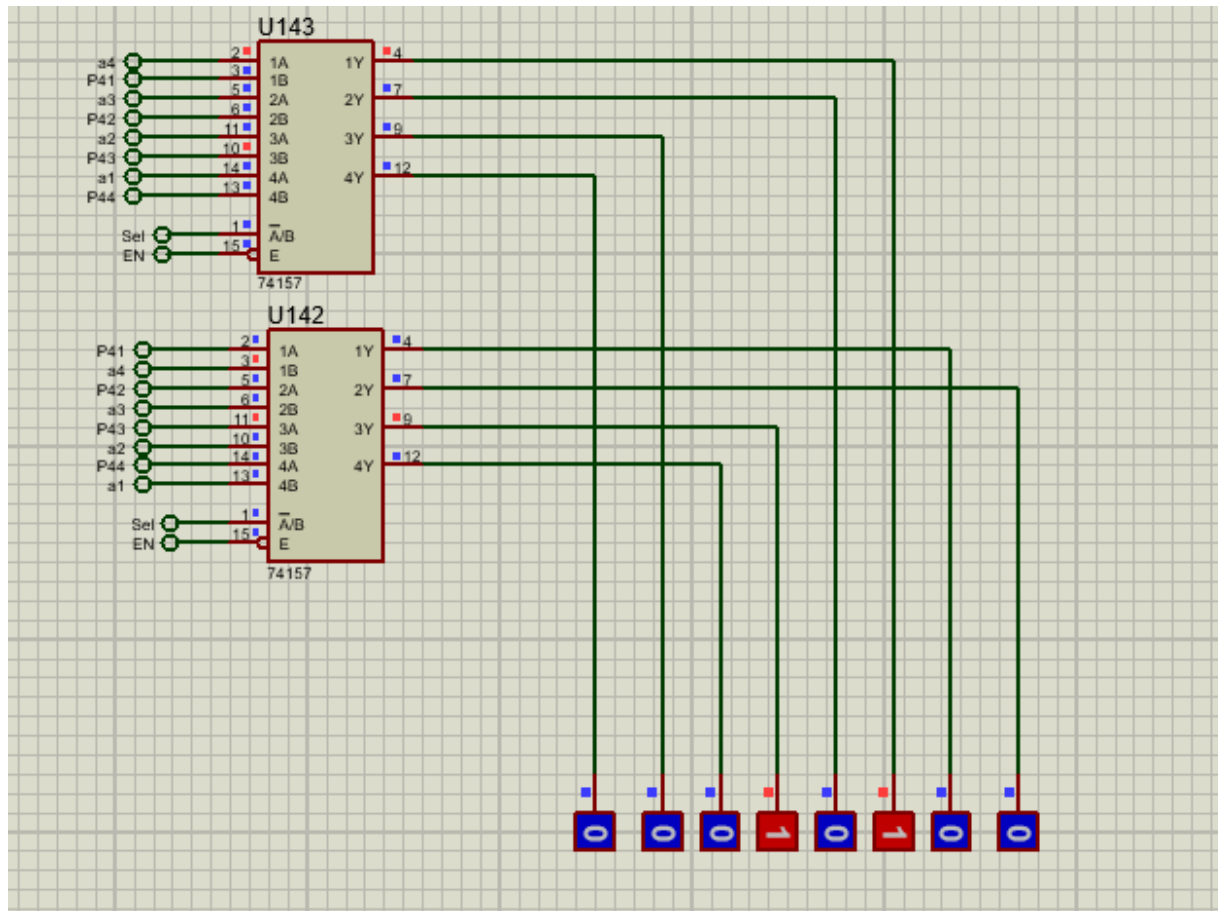
- This part of the circuit is for multiplexing the 4 round keys according to decryption and encryption .
- Bit 0 for encryption and bit 1 for decryption



→ Output with permutations



Sequential Approach

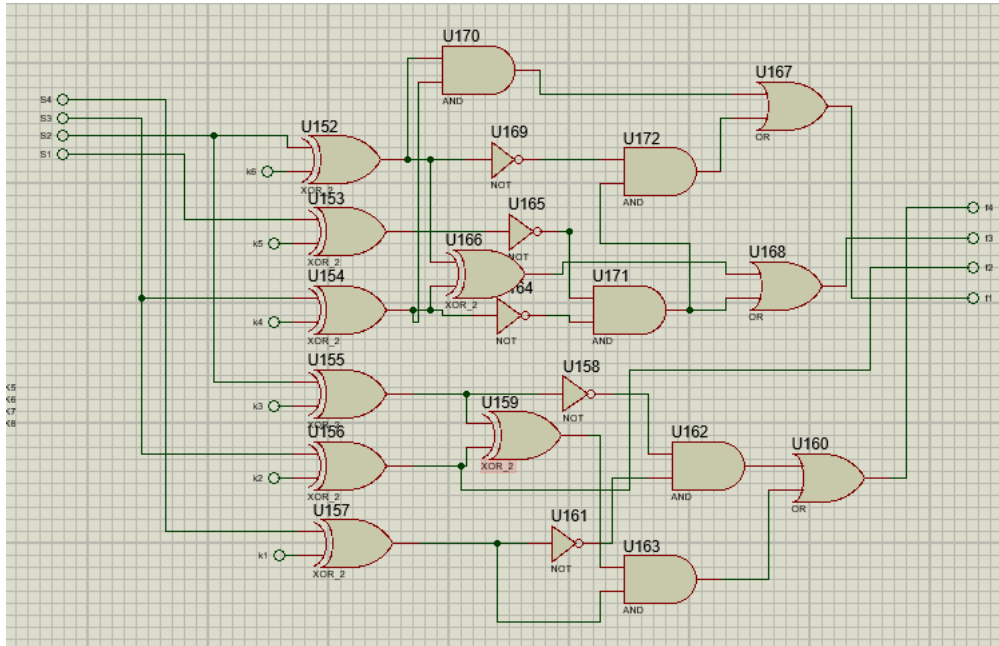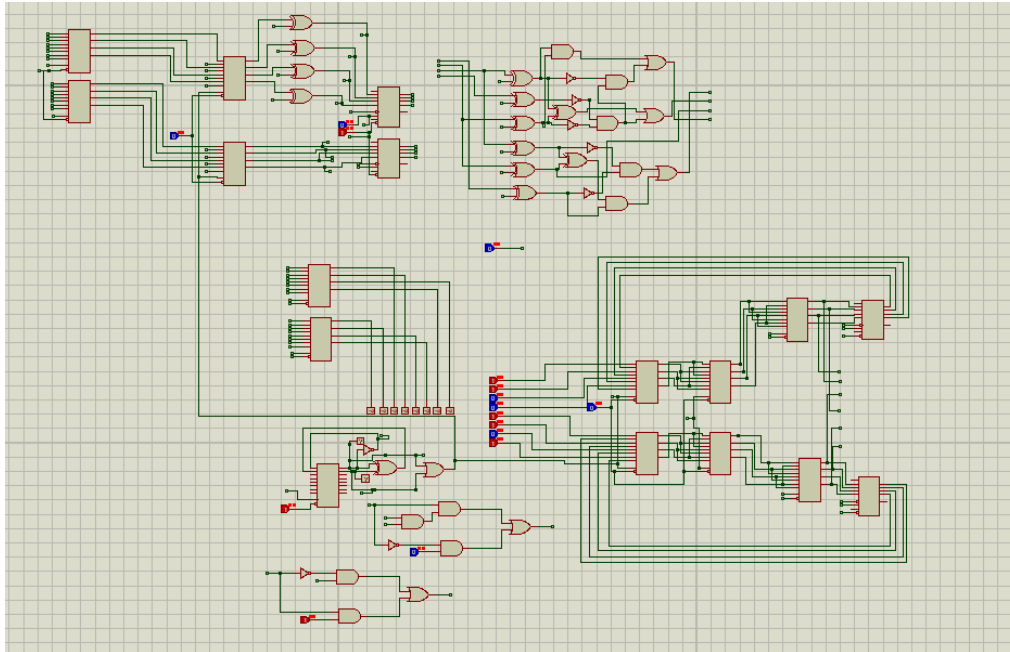→ The Input for both sequential and combinational circuit is same .




→ This part is for the function between the 6 bit round key and 4 bit LSB .

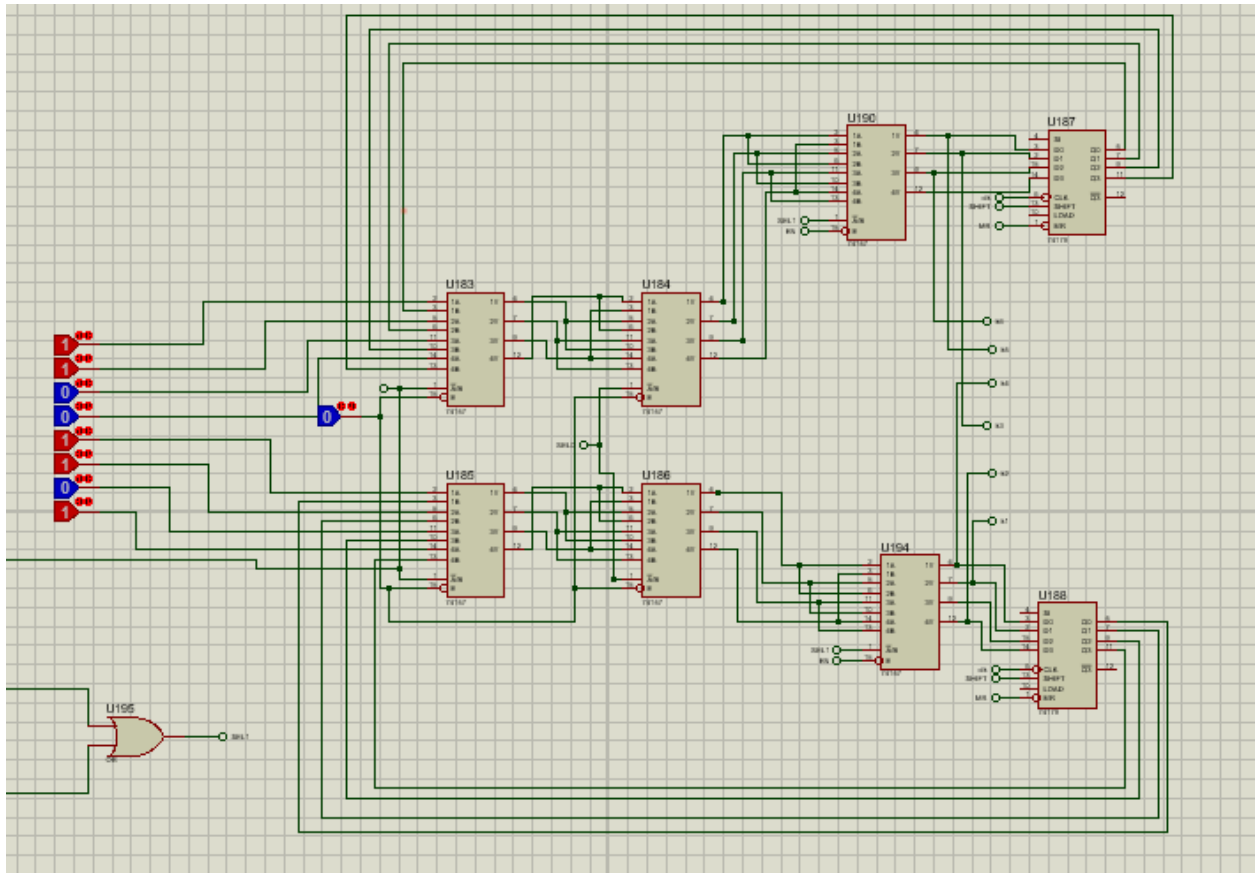 
→ This is for clk . And for running the sequential circuit we have to toggle rising 3 times after running the simulation




→ This part is for round key generating

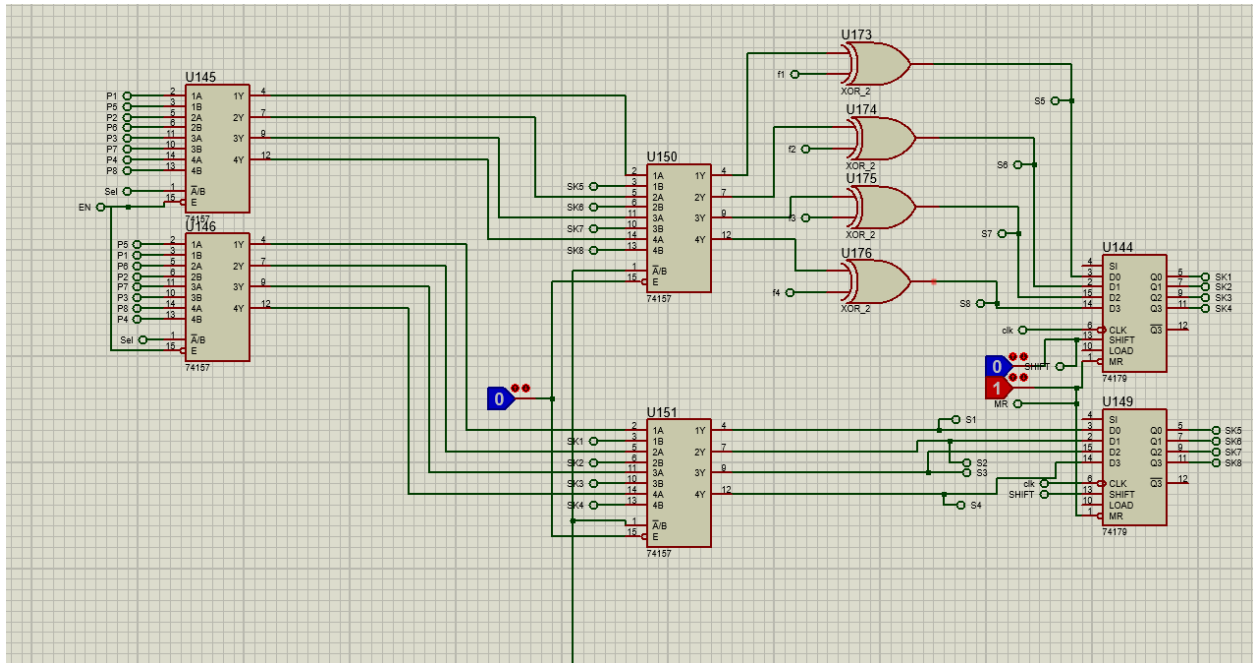

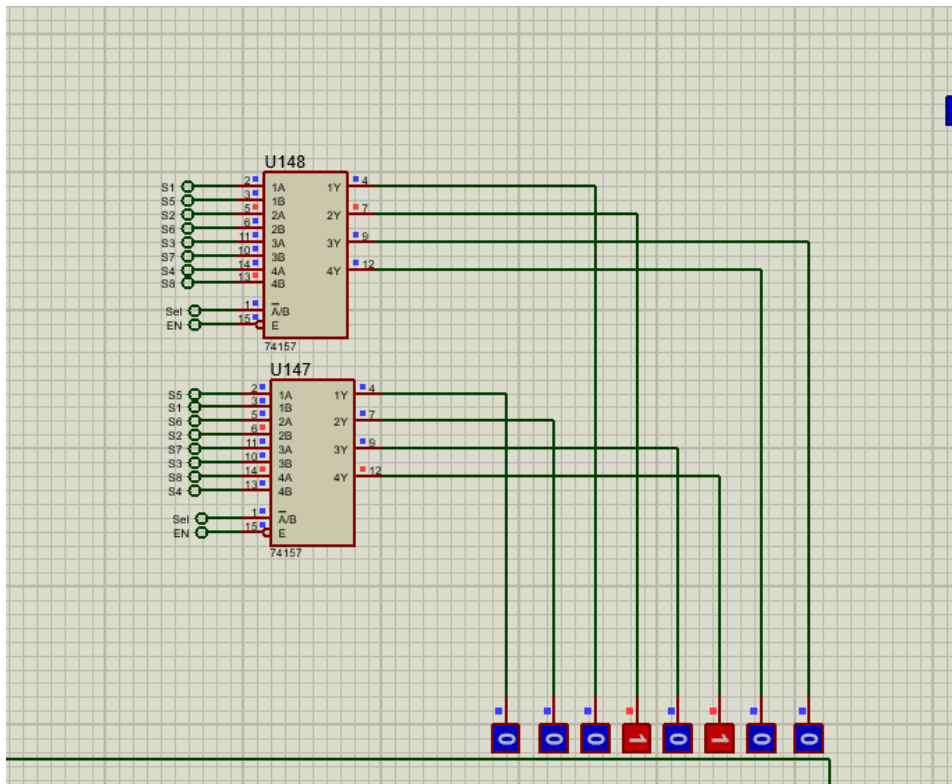
→ This part is for to get every round of 8 bit text data



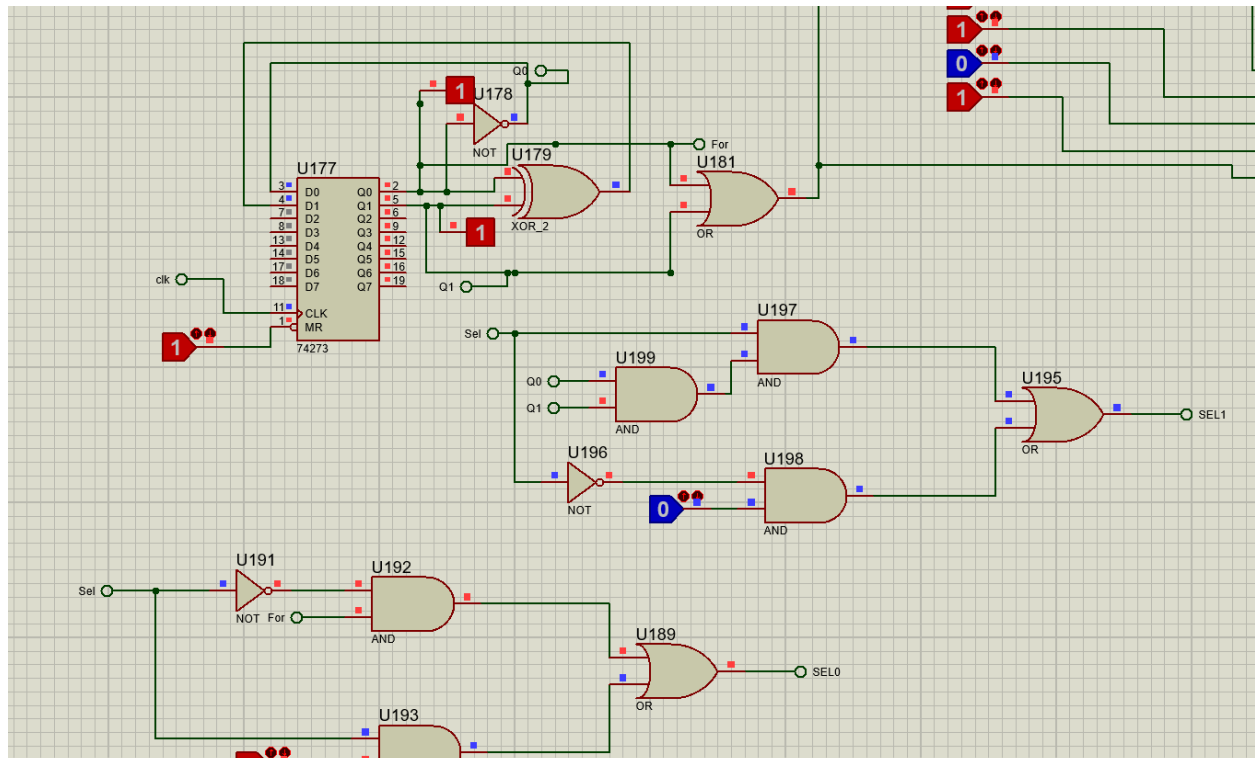→ This is output after three clock cycles



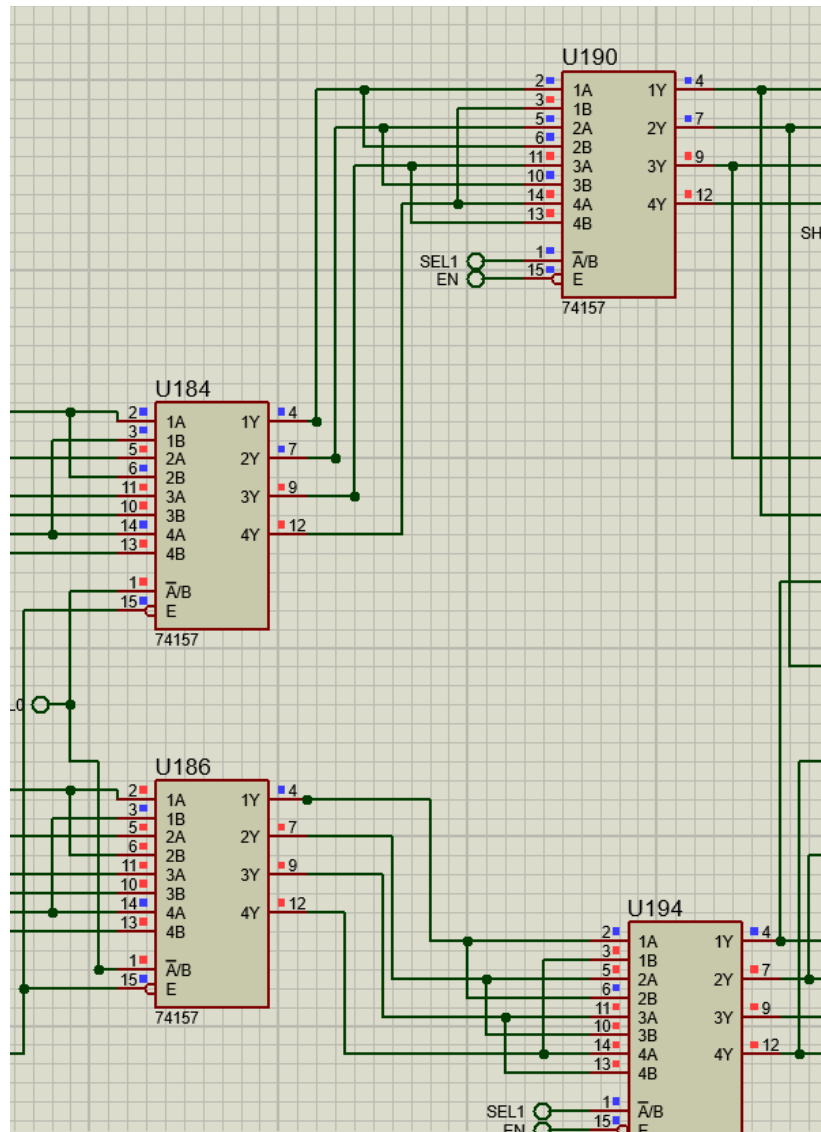→ This part is for generating control signals to get desired shifting of bits



→ This is a kind of Barrel shifter which shifts differently in different cycles .